ANSWER KEY

InquiryMind
LEARN · PLAY · WONDER

FACT CHECK · C4 · ELECTRICITY


Circuit facts

★☆☆
Grade 1


Learning goals

- Name circuit parts.
- Spot complete circuits.

1 Will the lamp light? Write yes or no.

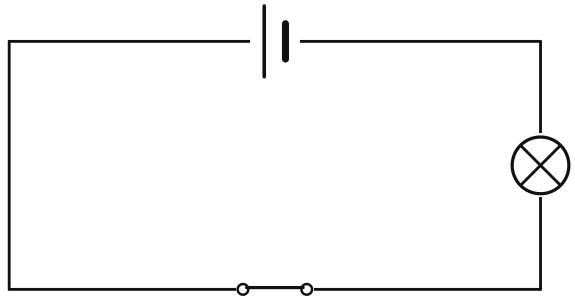

A

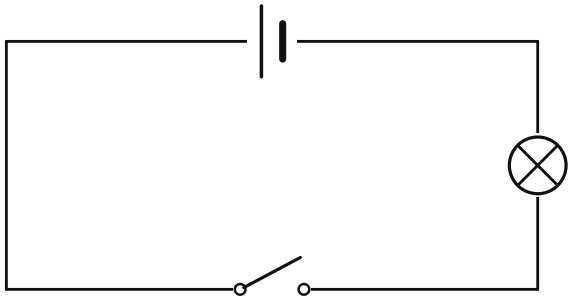

B

A	B
yes	no

2 Match the part to its job.

Draw a line to match each pair, or write the letter.

cell ●	→ A	● **A** pushes electricity round
wire ●	→ C	● **B** turns it on and off
switch ●	→ B	● **C** carries electricity
lamp ●	→ D	● **D** gives light

ANSWER KEY

InquiryMind
LEARN · PLAY · WONDER

THINK IT THROUGH · C4 · ELECTRICITY

Safe or not safe?

★★☆
Grade 1

Learning goals

- Think about electrical safety.

1 Sort these.

SORT THESE

using a torch with batteries **asking an adult to plug in**
touching a switch with wet hands **poking a socket**

Safe	Not safe
using a torch with batteries	poking a socket
asking an adult to plug in	touching a switch with wet hands

2 Why does the lamp go out when you open the switch?

There is a gap, so electricity cannot flow round the loop.

ANSWER KEY

InquiryMind
LEARN · PLAY · WONDER

INVESTIGATE · C4 · ELECTRICITY

Make a circuit

★★☆
Grade 1

Learning goals

- Build a circuit.
- Find out what makes it work.

You will need

a cell (battery), two wires with clips, a small bulb in a holder, a switch.

Join the cell, wires and bulb in a loop. Then add the switch.

1 Draw your circuit.

My circuit

A loop: cell → wire → switch → wire → bulb → back to the cell.

2 What happened when you took one wire off?

The bulb went out: the circuit was not complete.

ANSWER KEY

InquiryMind
LEARN · PLAY · WONDER

REAL-WORLD CASE STUDY · C4 · ELECTRICITY

Light from the sun

★★★
Grade 1

Learning goals

- Read about solar electricity.

Shuvo lives on a char, an island in a big river. There are no electricity wires there.

His family has a **solar panel** on the roof. In the day it turns sunlight into electricity and stores it in a battery. At night the battery lights two lamps, so Shuvo can do his homework.

1 **Where does Shuvo's electricity come from?**

● **the Sun** ○ a wall socket far away

2 **Why is a solar panel useful on the char?**

There are no electricity wires, but there is sunshine.

ANSWER KEY

InquiryMind
LEARN · PLAY · WONDER

REVIEW AND CHALLENGE · C4 · ELECTRICITY

Show what you know

★★★
Grade 1

Learning goals

- Use electricity words.

1 Find the words.

E	G	L	A	M	P	C
P	P	I	B	A	G	H
L	N	U	D	B	B	S
S	O	C	E	L	L	W
U	L	O	I	L	G	I
N	V	T	P	S	I	R
K	F	N	L	I	U	E

cell lamp loop sun wire

2 A lamp lights when the circuit is...

● **complete** ○ broken